



Verilog Tutorial


Adopted from

- Abdul-Rahman Elshafei's slides
- Digital Design, 4th Edition, Morris Mano, Micheal Ciletti



Motivation

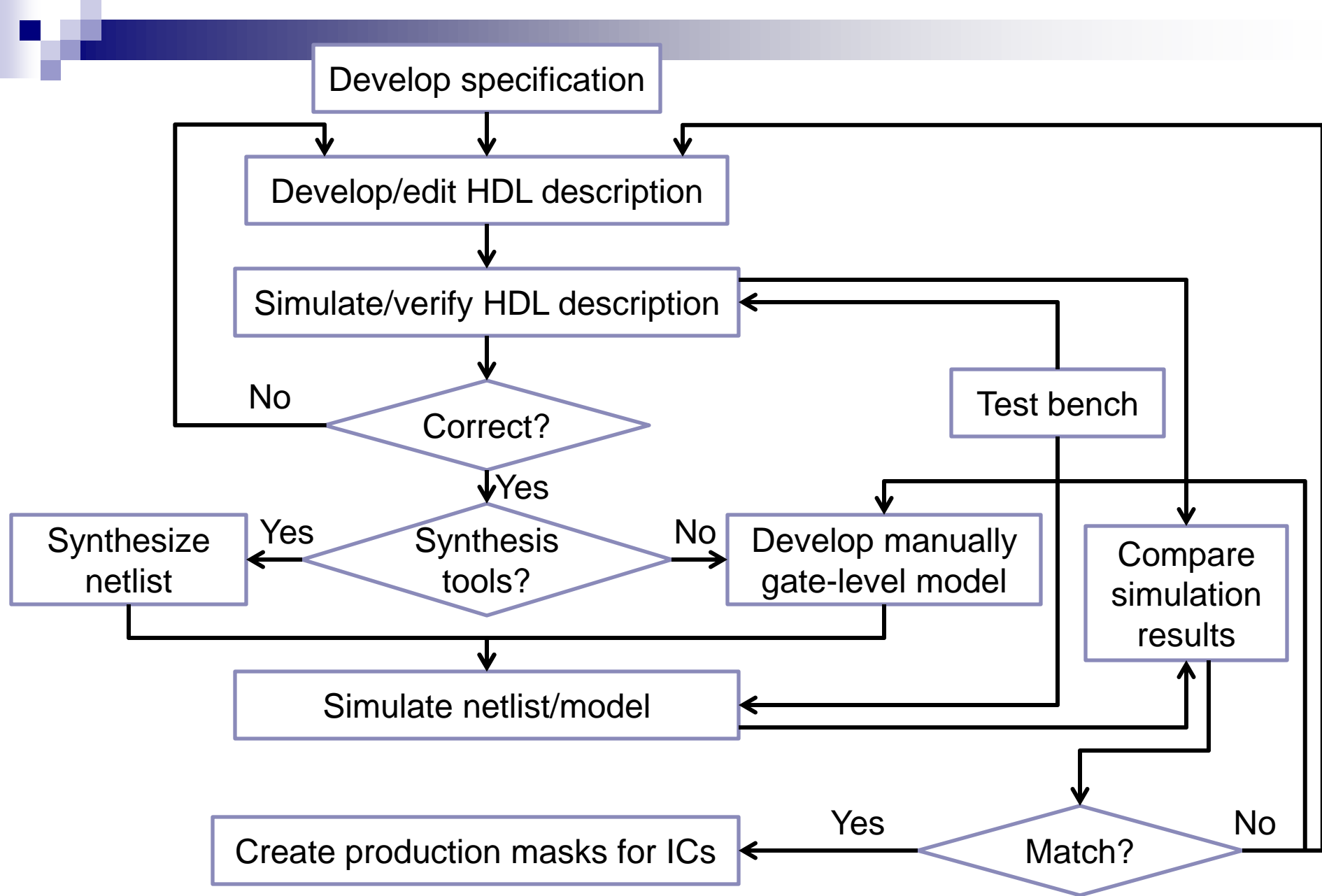
- Manual design methods are feasible for small logic circuits
- Modern design tools depend on a hardware description language (HDL)
- An HDL resembles an ordinary programming language but it is used to **describe**, **design** and **test** a circuit before manufacturing it



A simplified flow chart of HDL-based modeling, simulation and synthesis


Verilog Structure

 - All code are contained in modules
- Can invoke other modules
- Modules cannot be contained in another module
- A Verilog model is a descriptive model



```
module gate(Z,A,B,C);  
input A,B,C;  
output Z;  
assign Z = A|(B&C);  
endmodule
```
 
```
module two_gates(Z2,A2,B2,C2)  
input A2,B2,C2;  
output Z2;  
gate gate_1(G2,A2,B2,C2);  
gate gate_2(Z2,G2,A2,B2);  
endmodule
```



Lexicography

■ Comments:

Two Types:

- *// Comment*
- */* These comments extend over multiple lines. Good for commenting out code */*

■ Character Set:

0123456789ABCD..YZabcd...yz_\$

Identifiers cannot start with a number or \$

Data values for a single bit: 0,1,x,z

- x: an unknown value
- z: a high impedance
 - A high impedance condition occurs
 - at the output of three stage gates that are not enabled
 - if a wire is left unconnected

Truth table for predefined primitive **and** gate

and	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

Data Types

■ wire

- Used for connecting two points.
- Used in structural code
- Synthesizes into wires

■ reg

- Used for storing values.
- Used in procedural code
- May synthesize into latches, flip-flops or wires

■ integer

32-bit integer used as indexes

■ input, output, inout

Defines ports of a module (wire by default)

```
module sample (a,b,c,d);
```

```
input a,b;
```

```
output c,d;
```

```
wire [7:0] b;
```

```
reg c,d;
```


```
integer k;
```

Vectors and arrays: declaration


// An 8-bit vector
reg [7:0] Areg;



 
// A memory of 8 one-bit elements
reg Amem [7:0];



 
// A two-dimensional memory of one-bit elements
reg Bmem [7:0] [0:3];



 // A memory of four 8-bit words
reg [7:0] Cmem[0:3];



 // A two-dimensional memory of 3-bit elements
reg[2:0] Dmem [0:3] [0:4];




Vectors and arrays: selection


```
// declaration: reg [7:0] Areg;  
Areg [7:5]
```



 
```
// declaration: reg Amem [7:0];  
Amem [3]
```



 
```
// declaration: reg Bmem [7:0][0:3]  
Bmem [2] [1]
```


 
```
// declaration: reg[7:0] Cmem [0:3]  
Cmem [1] [6 -: 4]
```


 
```
// declaration: reg [2:0] Dmem [0:3][0:4]  
Dmem [0] [2]
```



Data Values

■ Numbers:

Numbers are defined by number of bits

Value of 23:

5'b10111

5'd23

5'h17

■ Constants:

```
wire [3:0] t,d;
```

```
assign t = 23;
```

```
assign d= 4'b0111;
```

■ Parameters:

```
parameter n=4;
```

```
wire [n-1:0] t, d;
```

```
`define Reset_state = 0, state_B =1,  
        Run_state =2, finish_state = 3;
```

```
if(state==`Run_state)
```

Operators

■ Arithmetic:

- ☐ * (multiplication)
- ☐ + (addition)
- ☐ - (subtraction)
- ☐ / (division)
- ☐ % (modulus)

■ Relational

- ☐ < (less than)
- ☐ <= (less than or equal)
- ☐ > (greater than)
- ☐ >= (greater than or equal)
- ☐ == (equality)
- ☐ != (inequality)

```
reg [3:0] a, b, c, d;  
wire[7:0] x,y,z;  
parameter n =4;
```

```
c = a + b;  
d = a * n;
```

```
if (x==y) d = 1; else d =0;
```

```
d = a ~^ b;
```

```
if ((x>=y) && (z)) a=1;  
    else a = !x;
```

Operators

■ Bit-wise Operators

- Not: ~
- XOR: ^
- And : & `5'b11001 & 5'b01101 ==> 5'b01001`
- OR: |
- XNOR: ~^ or ^~

■ Logical Operators

Returns 1 or 0, treats all nonzero as 1

- ! : Not
- && : AND `27 && -3 ==> 1`
- || : OR

```
reg [3:0] a, b, c, d;  
wire[7:0] x,y,z;  
parameter n =4;
```

```
c = a + b;  
d = a * n;
```

```
if (x==y) d = 1; else d =0;
```

```
d = a ~^ b;
```

```
if ((x>=y) && (z)) a=1;  
else a = !x;
```

Operators

■ Reduction Operators:

Unary operations returns single-bit values

- **&** : and
- **|** :or
- **~&** : nand
- **~|** : nor
- **^** : xor
- **~^** :xnor

■ Shift Operators

Shift Left: <<

Shift right: >>

■ Concatenation Operator

{ } (concatenation)

{ n{item} } (n fold replication of an item)

■ Conditional Operator

Implements if-then-else statement

(cond) ? (result if cond true) : (result if cond false)

```
module sample (a, b, c, d);  
input [3:0] a, b;  
output [3:0] c, d;  
wire z,y,carry;
```

```
assign z = ~| a;  
c = a * b;  
if (a==b) d = 1; else d =0;
```

```
d = a ~^ b;
```


```
if ((a>=b) && (z)) y=1;  
else y = !x;
```

```
assign c=d << 2; //shift left twice  
assign {carry, d} = a + b;  
assign c = {2{carry},2{1'b0}};  
// c = {carry,carry,0,0}
```


```
assign c = (inc==2)? a+1:a-1;
```

Concatenation example
 
```
1 module bus_con (a,b);  
2     input  [3:0] a, b;  
3     output [7:0] y;  
4     wire  [7:0] y;  
5  
6     assign y = {a,b};  
7  
8 endmodule
```



The best way to describe a circuit?

 

$$I_{out} = (\overline{I \oplus Q})(I \oplus I_{prev} + (I \oplus Q)(Q \oplus Q_{prev}))$$

$$Q_{out} = (\overline{I \oplus Q})(Q \oplus Q_{prev} + (I \oplus Q)(I \oplus I_{prev}))$$

(I, Q) prev)					
IQ		00	01	11	10
		00	01	11	10
00		00	01	11	10
01		10	00	01	11
11		11	10	00	01
10		01	11	10	00
		Iout, Qout			

- If both inputs are 1, change both outputs.
- If one input is 1 change an output as follows:
 - If the previous outputs are equal change the output with input 0;
 - If the previous outputs are unequal change the output with input 1.
- If both inputs are 0, change nothing.

Structural vs Procedural

Structural

- Textual description of circuit
- Order does not matter
- Starts with **assign** statements
- Harder to code
- Need to work out logic

Procedural

- Think like C code
- Order of statements are important
- Starts with **initial** or **always** statement
- Easy to code
- Can use case, if, for

Structural vs Procedural

assign statement

- **assign** $Y = (A \& S) | (B \& \sim S);$
- continuous assignment statement
- executes whenever the value of the expression on the right hand side changes
- represents a combinational circuit


Structural vs Procedural

always statement

- **always @(event control expression)**
begin
// Procedural assignment statements that execute
// when the condition is met
end
- has a cyclic behavior
- In one of the forms:
 - Level sensitive: **always @(A or B or C)**
 - Edge sensitive: **always @(posedge clock or negedge reset)**


Structural
 
```
wire [3:0] Q;  
wire [1:0] y;  
assign Q[0]=(~y[1])&(~y[0]);  
assign Q[1]=(~y[1])&y[0];  
assign Q[2]=y[1]&(~y[0]);  
assign Q[3]=y[1]&y[0];
```



Procedural
 
```
reg [3:0] Q;  
wire [1:0] y;  
always@(y)  
begin  
    Q=4'b0000;  
    case(y)  
    begin  
        2'b00: Q[0]=1;  
        2'b01: Q[1]=1;  
        2'b10: Q[2]=1;  
        2'b11: Q[3]=1;  
    endcase  
end
```



Structural vs Procedural

Structural

- Textual description of circuit
- Order does not matter
- Starts with **assign** statements
- Harder to code
- Need to work out logic

Procedural

- Think like C code
- Order of statements are important
- Starts with **initial** or **always** statement
- Easy to code
- Can use case, if, for

Blocking vs Non-Blocking assignment

Blocking

- `<variable> = <statement>`
- Similar to C code
- The next assignment waits until the present one is finished
- Used for combinational logic

Non-blocking

- `<variable> <= <statement>`
- The inputs are stored once the procedure is triggered
- Statements are executed in parallel
- Used for flip-flops, latches and registers



Do not mix both assignments in one procedure

Blocking vs Non-Blocking assignment

```
B = A  
C = B+1  
// sets C to A+1
```

```
B <= A  
C <= B+1  
// sets C the original value of B+1
```



Behavior Modeling

if Statements

Syntax

```
if (expression)  
begin  
    ...statements...  
end
```

```
else if (expression)  
begin  
    ...statements...  
end  
    ...more else if blocks
```

```
else  
begin  
    ...statements...  
end
```

```
if (alu_func == 2'b00)  
    aluout = a + b;  
else if (alu_func == 2'b01)  
    aluout = a - b;  
else if (alu_func == 2'b10)  
    aluout = a & b;  
else // alu_func == 2'b11  
    aluout = a | b;
```


case Statements

Syntax

```
case (expression)
  case_choice1:
```

```
  begin
```

```
    ...statements...
```

```
  end
```

```
  case_choice2:
```

```
  begin
```

```
    ...statements...
```

```
  end
```

```
  ...more case choices blocks...
```

```
  default:
```

```
  begin
```

```
    ...statements...
```

```
  end
```

```
endcase
```

```
case (alu_ctr)
```

```
  2'b00: aluout = a + b;
```

```
  2'b01: aluout = a - b;
```

```
  2'b10: aluout = a & b;
```

```
  default: aluout = 1'bx; // Treated as don't cares for  
endcase // minimum logic generation.
```

for loops

Syntax

```
for (count= value1;  
    count<,<=,>,>= value2;  
    count=count +,- step)  
begin  
    ...statements...  
end
```


```
integer j;  
  
for(j=0;j<=7;j=j+1)  
begin  
    c[j] = a[j] + b[j];  
end
```



Component Inference


Flip-Flops
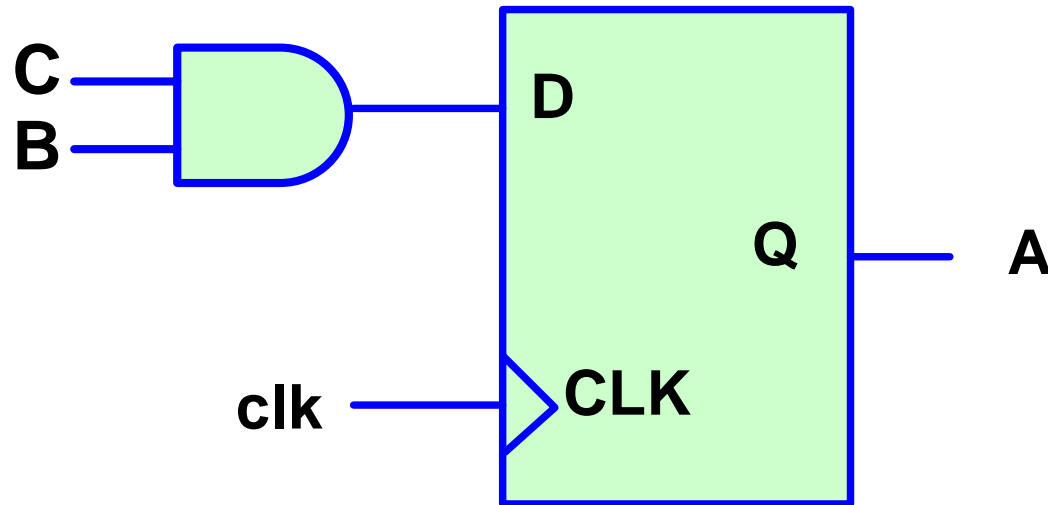
```
module ff(b, c, clk, a);  
  input b,c,clk;  
  output a;  
  reg a;  
  always@(posedge clk)  
  begin  
    a<=b&c;  
  end  
endmodule
```




D Flip-Flop with Asynchronous Reset
 
```
always@(posedge clk or  
    negedge rst)  
begin  
    if (!rst) a<=0;  
    else a<=b;  
end
```




D Flip-flop with Synchronous reset and Enable
 
```
always@(posedge clk)
begin
    if (rst) a<=0;
    else if (enable) a<=b;
end
```



Shift Registers
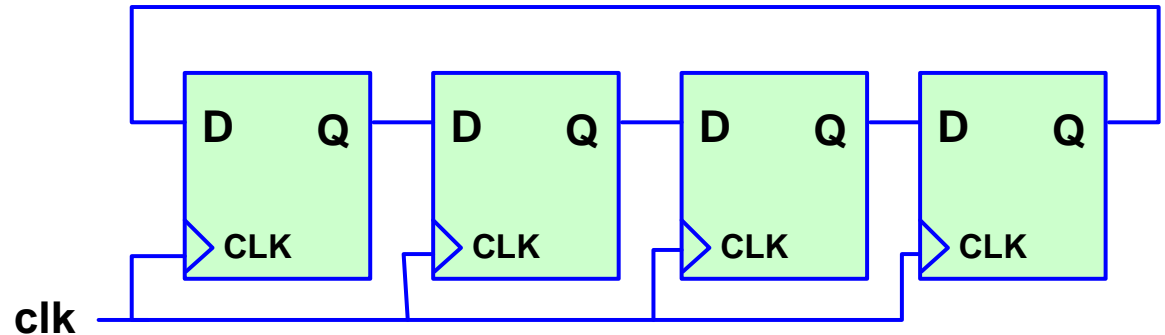
```
reg[3:0] Q;  
always@(posedge clk or  
posedge rset )  
begin  
  if (rset) Q<=0;  
  else begin  
    Q[3:1]<=Q[2:0];  
    Q[0]<=Q[3];  
  end
```



Multiplexers

Method 1


assign a = (select ? b : c);

Method 2

```
always@(select or b or c) begin
    if(select) a=b;
    else a=c;
end
```


Method 2b
 
```
always@(select or b or c) begin
    case(select)
        1'b1: a=b;
        1'b0: a=c;
    endcase
end
```



Counters
 
```
reg [7:0] count;
wire enable;
always@(posedge clk or
        posedge rst)
begin
    if (rst) count<=0;
    else if (enable)
        count<=count+1;
end
```





Avoiding Unwanted Latches

Latches are BAD

Inferred latches


- If no care is taken, compiler can infer latches in your combinational circuits

□ not a combinational circuit anymore!

```
module synInferredLatch
  (output reg f,
   input      a, b, c);

  always @(*)
    if (a == 1)
      f = b & c;

endmodule
```

 

Rule #1



**If the procedure has several paths,
every path must evaluate all outputs**

■ Method1:

Set all outputs to some value at the start of the procedure.

Later on different values can overwrite those values.

always @(...

begin

 x=0;y=0;z=0;

if (a) x=2; **elseif** (b) y=3; **else** z=4;

End

■ Method2:

Be sure every branch of every if and case generate every output

always @(...

begin

if (a) begin x=2; y=0; z=0; end

elseif (b) begin x=0; y=3; z=0; end

else begin x=0; y=0; z=4; end

end

Rule #2



All inputs used in the procedure must appear in the trigger list

- **Right-hand side variables:**

Except variables both calculated and used in the procedure.

always @(a or b or c or ~~x or y~~)

begin

 x=a; y=b; z=c;

 w=x+y;

end

Rule #3



All possible inputs used to control statements must be covered

- End all case statements with the default case whether you need it or not.

```
case(state)
```

```
...
```

```
default: next_state = reset;
```

```
endcase
```

- Do not forget the self loops in your state graph

```
if(a|b&c) next_state=S1;
```

```
elseif(c&d) next_state=S2;
```

```
else next_state=reset;
```



Finite State Machines

Standard Form for a Verilog FSM

// state flip-flops

```
reg [2:0] state, next_state;
```

// state definitions

```
parameter
```

```
    reset=0,S1=1,S2=2,S3=3,..
```

// NEXT STATE CALCULATIONS

```
always@(state or inputs or ...)
```

```
begin
```

```
    ...
```

```
    next_state= ...
```

```
    ...
```

```
end
```

// REGISTER DEFINITION

```
always@(posedge clk)
```

```
begin
```

```
    state<=next_state;
```

```
end
```

// OUTPUT CALCULATIONS

```
output= f(state, inputs)
```


Example

```
module myFSM (clk, x, z)
input clk, x; output z;

// state flip-flops
reg [2:0] state, nxt_st;
// state definition
parameter S0=0,S1=1,S2=2,S3=3,S7=7

// REGISTER DEFINITION
always @(posedge clk)
begin
    state<=nxt_st;
end

// OUTPUTCALCULATIONS
assign z = (state==S7);
```

```
// NEXT STATE CALCULATIONS
always @(state or x)
begin
case (state)
    S0: if(x) nxt_st=S1;
        else nxt_st=S0;
    S1: if(x) nxt_st=S3;
        else nxt_st=S2;
    S2: if(x) nxt_st=S0;
        else nxt_st=S7;
    S3: if(x) nxt_st=S2;
        else nxt_st=S7;
    S7:  nxt_st=S0;
    default: nxt_st = S0;
endcase
end

endmodule
```

Test Benches



System tasks

- Used to generate input and output during simulation. Start with \$ sign.

- Display Selected Variables:

\$display ("format_string",par_1,par_2,...);

\$monitor("format_string",par_1,par_2,...);

Example: **\$display**("Output z: %b", z);

- Query current simulation time: **\$time**



Test Benches

Overview

1. Invoke the verilog under design
2. Simulate input vectors
3. Implement the system tasks to view the results

Approach

1. Initialize all inputs
2. Set the clk signal
3. Send test vectors
4. Specify when to end the simulation.

Example

```
'timescale1 ns /100 ps
// timeunit =1ns; precision=1/10ns;
module my_fsm_tb;
reg clk, rst, x;
wire z;

/**** DESIGN TO SIMULATE (my_fsm)
    INSTANTIATION ****/
myfsm dut1(clk, rst, x, z);

/****RESET AND CLOCK SECTION****/
Initial
begin
clk=0;
rst=0;
#1rst=1; /*The delay gives rst a posedge for
    sure.*/
#200 rst=0; //Deactivate reset after two clock
    cycles +1ns*/
end
always #50clk=~clk; /* 10MHz clock (50*1ns*2)
    with 50% duty-cycle */
```

```
/****SPECIFY THE INPUT WAVEFORM x ****/
Initial begin
$monitor("Time: %d Output z: %b", $time, z);
#1 x=0;
#400 x=1;
$display("Output z: %b", z);
#100 x=0;

#1000 $finish; //stop simulation
//without this, it will not stop
end
endmodule
```

One last slide





Coding guidelines

- Don't mix level and edge sensitive elements in the same always block
- Avoid mixing positive and negative edge-triggered flip-flops
- Use continuous assign statements for simple combinational logic
- Use nonblocking for sequential and blocking for combinational logic
- Don't mix blocking and nonblocking assignments in the same always block
- Be careful with multiple assignments to the same variable
- Define all if-else or case statements explicitly